



RC5

ECE3110J Analog Circuits

Kezhi Li
2024 Summer




上海交通大學
SHANGHAI JIAO TONG UNIVERSITY


MOSFET Basics



NMOS

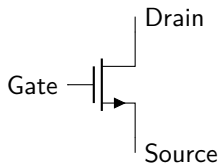

PMOS

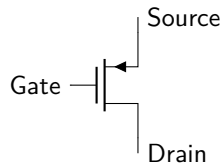

I-V Characteristics (NMOS)



When $V_{DS} < V_{GS} - V_{TH}$, the NMOS is in triode region.

$$I_D = \mu_n C_{ox} \frac{W}{L_{eff}} \left[(V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right] \quad (1)$$

When $V_{DS} \geq V_{GS} - V_{TH}$, the NMOS is in saturation region.

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L'} (V_{GS} - V_{TH})^2 \quad (2)$$

I-V Characteristics (PMOS)



When $V_{SD} < V_{SG} - |V_{TH}|$, the PMOS is in triode region.

$$I_D = \mu_p C_{ox} \frac{W}{L_{eff}} \left[(V_{SG} - |V_{TH}|) V_{SD} - \frac{1}{2} V_{SD}^2 \right] \quad (3)$$

When $V_{SD} \geq V_{SG} - |V_{TH}|$, the NMOS is in saturation region.

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L'} (V_{SG} - |V_{TH}|)^2 \quad (4)$$

Second Effects



Channel-Length Modulation

$$L' = L_{\text{eff}} - \Delta L \quad (5)$$

$$\begin{aligned} I_D &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{\text{eff}}} (V_{GS} - V_{TH})^2 \left(1 + \frac{\Delta L}{L_{\text{eff}}} \right) \\ &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{\text{eff}}} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}) \end{aligned} \quad (6)$$

Body Effect

$$V_{TH} = V_{TH0} + \gamma (\sqrt{|2\Phi_F + V_{SB}|} - \sqrt{|2\Phi_F|}) \quad (7)$$

$$g_{mb} = g_m \cdot \eta, \eta = \frac{\gamma}{2\sqrt{|2\Phi_F + V_{SB}|}} \quad (8)$$

Transconductance



$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L'} (V_{GS} - V_{TH}) = \sqrt{2\mu_n C_{ox} \frac{W}{L'} I_D} = \frac{2I_D}{V_{GS} - V_{TH}} \quad (9)$$


With channel-length modulation:

$$\begin{aligned} g_m &= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) (1 + \lambda V_{DS}) \\ &= \sqrt{2\mu_n C_{ox} (W/L) I_D} (1 + \lambda V_{DS}) \end{aligned} \quad (10)$$

Small-Signal Model for NMOS



$$\lambda \neq 0, \gamma = 0$$

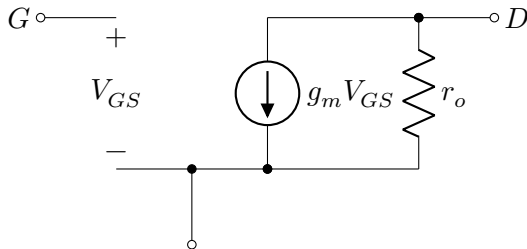


Where,

$$r_o = \frac{1}{\partial I_D / \partial V_{DS}} = \frac{1}{\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \cdot \lambda} \quad (11)$$


Small-Signal Model for NMOS



$$\lambda \neq 0, \gamma \neq 0$$

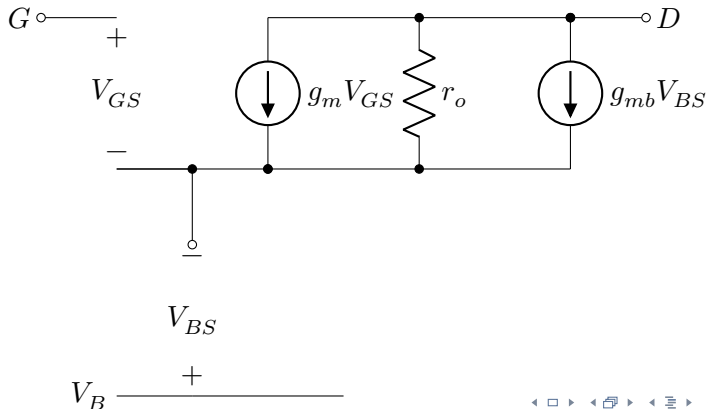


Common-Source with Resistive Load

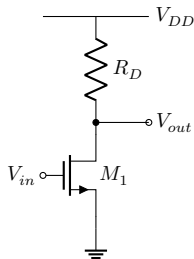


- Draw the curves of V_{out} vs V_{in} and write the corresponding relationship.
- Calculate the voltage gain $A_v = \frac{\partial V_{out}}{\partial V_{in}}$.
- What if $\lambda \neq 0$, $\gamma \neq 0$?

Common-Source with Resistive Load

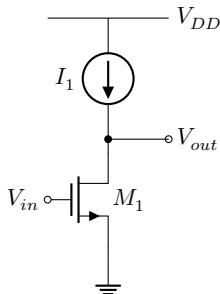

- Calculate the voltage gain $A_v = \frac{\partial V_{out}}{\partial V_{in}}$ if $\lambda \neq 0$, $\gamma \neq 0$.

Common-Source with Diode-Connected Load

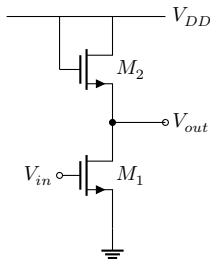

- Draw the curves of V_{out} vs V_{in} and write the corresponding relationship.
- How to compare it to resistive load?
- Calculate the voltage gain $A_v = \frac{\partial V_{out}}{\partial V_{in}}$.
- What if $\lambda \neq 0$, $\gamma \neq 0$?

Something to Talk about Midterm

