



# Lecture 17: Differential Amplifiers

VE 311 Analog Circuits

Xuyang Lu  
2024 Summer



上海交通大學  
SHANGHAI JIAO TONG UNIVERSITY

# Recap of Last Lecture



- Common Gate
- Cascode (Telescopic, Folded)
- Differential Amplifier (Current Equation, Superposition)

# Topics to be Covered





- Differential Amplifier (Half circuit method)
- More on differential amplifier topologies
- Current mirror
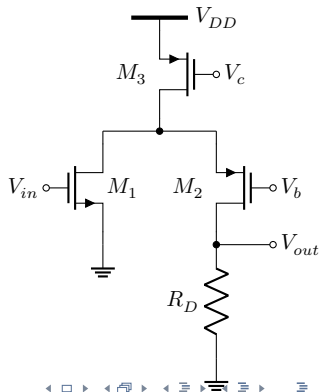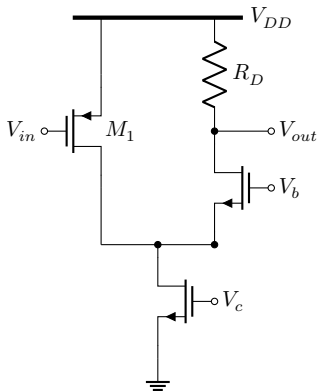
## Folded Cascode ( $\lambda \neq 0, \gamma \neq 0$ )



We don't care about  $M_3$ 's non-ideality.



## Folded Cascode ( $\lambda \neq 0, \gamma \neq 0$ )




$$G_m = -g_{m1} \frac{(r_{o1} \parallel r_{o3})}{(r_{o1} \parallel r_{o3}) + \left( r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \right)} \quad (1)$$

$$R_{out} = [(r_{o1} \parallel r_{o3}) + r_{o2} + (g_{m2} + g_{mb2})r_{o2}(r_{o1} \parallel r_{o3})] \parallel R_D \quad (2)$$

$$A_v = G_m R_{out} \quad (3)$$

# Differential-Mode (Superposition)

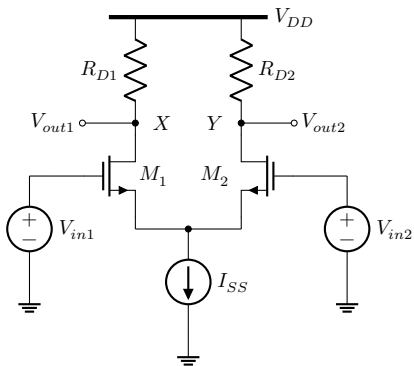



$$A_{DM} = \frac{V_{out1} - V_{out2}}{V_{in1} - V_{in2}} \quad (4)$$

$$= -g_m R_D \quad (5)$$

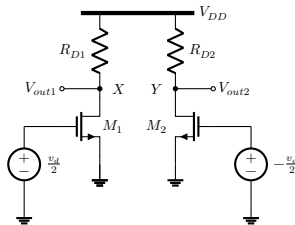
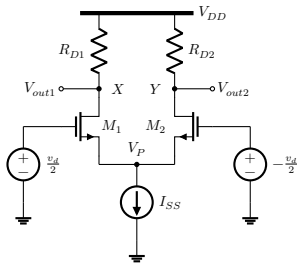
## Small-Signal, Half-circuit ( $\lambda \neq 0, \gamma \neq 0$ )



- Assume the circuit is fully symmetric.
- For  $i_{d1} + i_{d2} = 0$  and  $g_{m1} \frac{v_d}{2} + g_{m2}(-\frac{v_d}{2}) = 0$ ,  $V_P$  must be a constant voltage in DC analysis and a virtual ground in small-signal analysis.


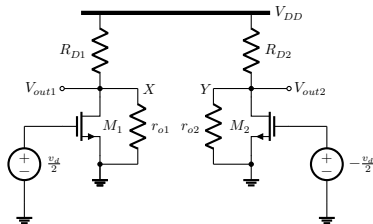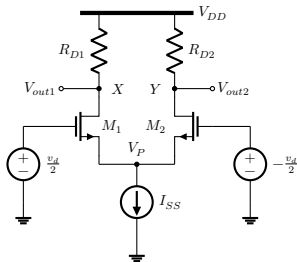
# Small-Signal, Half-circuit ( $\lambda \neq 0, \gamma \neq 0$ )



$$V_{out1} = -g_m(R_D \parallel r_o) \frac{v_d}{2} \quad (6)$$

$$V_{out2} = -g_m(R_D \parallel r_o) \left(-\frac{v_d}{2}\right) \quad (7)$$

$$A_{DM} = \frac{V_{out1} - V_{out2}}{v_d} = -g_m(R_D \parallel r_o) \quad (8)$$




## Common-Mode Response ( $\lambda \neq 0, \gamma \neq 0$ )





If the circuit is fully symmetric,

$$A_{CM-DM} = \frac{V_{out1} - V_{out2}}{v_{in,CM}} = 0 \quad (9)$$

$$CMRR = \left| \frac{A_{DM}}{A_{CM-DM}} \right| = \infty \quad (10)$$

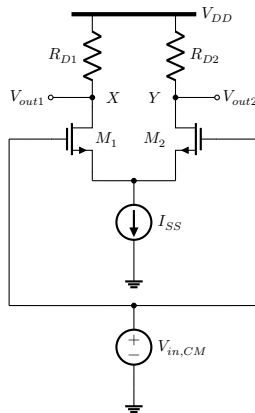
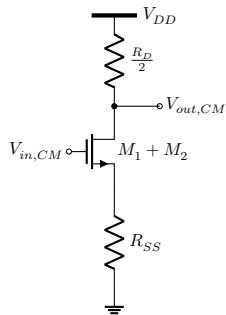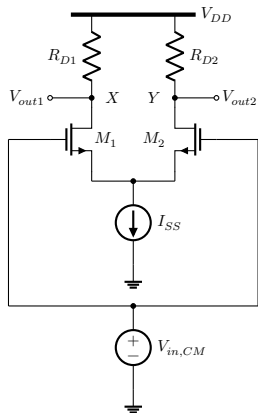
# Common-Mode Response ( $\lambda \neq 0, \gamma \neq 0$ )



Perturbing biasing condition  $\rightarrow$  Altering transconductance ( $g_m$ )

## Common-Mode Response ( $\lambda \neq 0, \gamma \neq 0$ )



If the circuit is fully symmetric,


$$A_{CM} = \frac{V_{out,CM}}{V_{in,CM}} \quad (11)$$

$$= \frac{-2g_m \frac{r_o}{2}}{R_{SS} + \frac{r_o}{2} + (2g_m + 2g_{mb2}) \frac{r_o}{2} R_{SS}} \cdot \frac{[R_{SS} + \frac{r_o}{2} + (2g_m + 2g_{mb}) \frac{r_o}{2} R_{SS}] \frac{R_D}{2}}{[R_{SS} + \frac{r_o}{2} + (2g_m + 2g_{mb}) \frac{r_o}{2} R_{SS}] + \frac{R_D}{2}} \quad (12)$$

$$= 0 \quad \text{if } R_{SS} = \infty \quad (13)$$



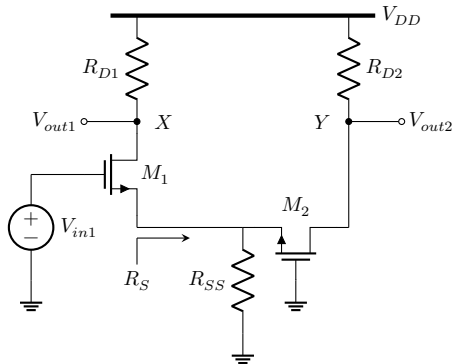
## Nonzero $R_{SS}$ ( $\lambda = 0, \gamma = 0$ )




$$R_S = \frac{1}{g_{m2}} \parallel R_{SS} \quad (14)$$
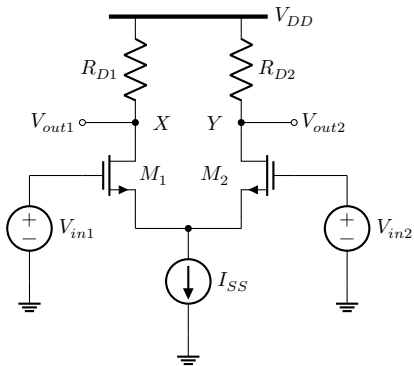
## Nonzero $R_{SS}$ ( $\lambda = 0, \gamma = 0$ )




$$V_{out1} = -\frac{R_D}{\frac{1}{g_{m1}} + \left(\frac{1}{g_{m2}} \parallel R_{SS}\right)} V_{in1} \quad (15)$$
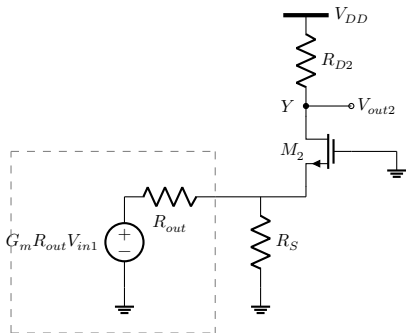
# Nonzero $R_{SS}$ ( $\lambda = 0, \gamma = 0$ )




$$G_m = g_{m1} \quad (16)$$
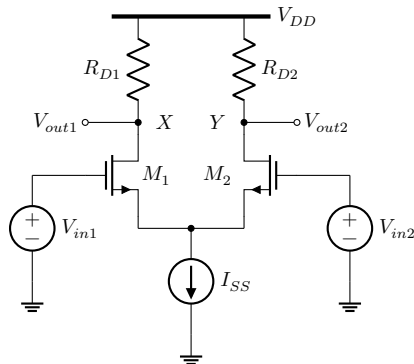
$$R_{out} = \frac{1}{g_{m1}} \quad (17)$$



$$V_{out2} = - \frac{\frac{R_{SS}}{R_{SS} + \frac{1}{g_{m2}}} R_D}{\frac{1}{g_{m1}} + \left( \frac{1}{g_{m2}} \parallel R_{SS} \right)} V_{in1} \quad (18)$$

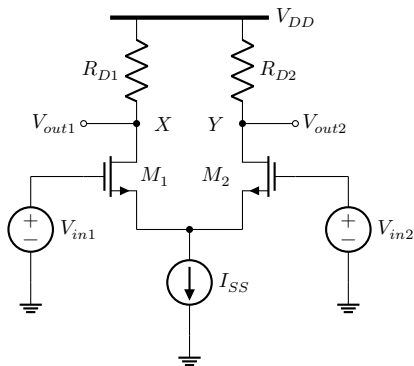Nonzero  $R_{SS}$ 


$$V_{out1} - V_{out2} = -\frac{(g_{m1} + 2R_{SS}g_{m1}g_{m2})R_D}{1 + (g_{m1} + g_{m2})R_{SS}}V_{in1} \quad (19)$$

$$= -g_m R_D V_{in1} \quad (20)$$

$$V_{out1} - V_{out2} = -\frac{(g_{m1} + 2R_{SS}g_{m1}g_{m2})R_D}{1 + (g_{m1} + g_{m2})R_{SS}}V_{in1} \quad (21)$$

$$= -g_m R_D V_{in2} \quad (22)$$

# Nonzero $R_{ss}$

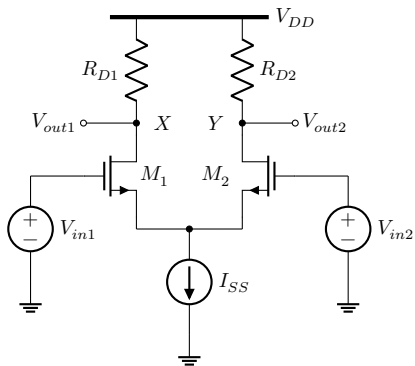

$$A_{DM} = \frac{V_{out1} - V_{out2}}{V_{in1} - V_{in2}} = -g_m R_D \quad (23)$$



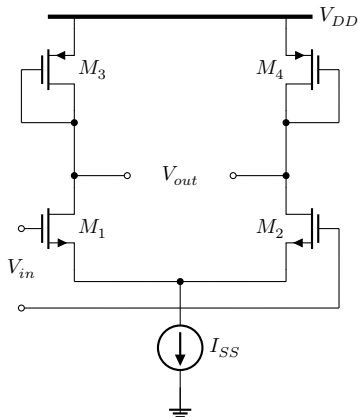
# $A_{DM}$ with MOS Loads ( $\lambda \neq 0, \gamma \neq 0$ )



Higher  $A_{DM}$

- $\rightarrow$  Smaller  $(W/L)_P$
- $\rightarrow$  Larger  $(V_{SGP} - V_{THP})$
- $\rightarrow$  Smaller  $V_{in,CM}$  headroom



## $A_{DM}$ with MOS Loads ( $\lambda \neq 0, \gamma \neq 0$ )




$$V_{out1} = -g_{mN}(r_{oN} \parallel r_{oP} \parallel \frac{1}{g_{mP}}) \frac{v_d}{2} \quad (24)$$

$$V_{out2} = -g_{mN}(r_{oN} \parallel r_{oP} \parallel \frac{1}{g_{mP}}) (-\frac{v_d}{2}) \quad (25)$$

$$A_{DM} = \frac{V_{out1} - V_{out2}}{v_d} = -g_{mN} \left( r_{oN} \parallel r_{oP} \parallel \frac{1}{g_{mP}} \right) \quad (26)$$

$$\approx -\frac{g_{mN}}{g_{mP}} \approx -\sqrt{\frac{\mu_n(W/L)_N}{\mu_p(W/L)_P}} \quad (27)$$
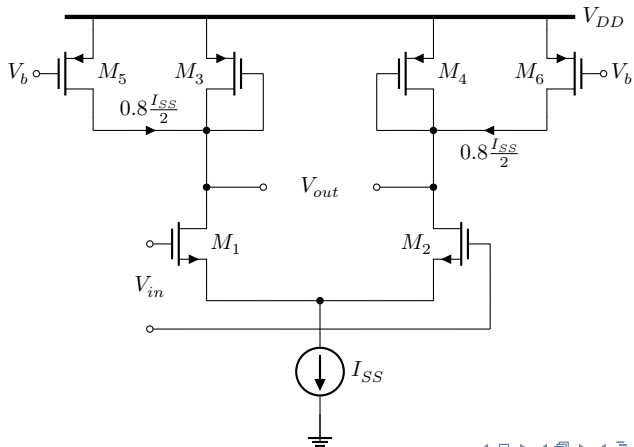
# $A_{DM}$ with MOS Loads ( $\lambda \neq 0$ , $\gamma \neq 0$ )



## $A_{DM}$ with MOS Loads



$$V_{out1} = -g_{m1,2} \left( r_{o1,2} \parallel r_{o3,4} \parallel \frac{1}{g_{m3,4}} \parallel r_{o5,6} \right) \frac{v_d}{2} \quad (28)$$

$$V_{out2} = -g_{m1,2} \left( r_{o1,2} \parallel r_{o3,4} \parallel \frac{1}{g_{m3,4}} \parallel r_{o5,6} \right) \left( -\frac{v_d}{2} \right) \quad (29)$$

$$A_{DM} = \frac{V_{out1} - V_{out2}}{v_d} \approx -\frac{g_{m1,2}}{g_{m3,4}} \approx -\sqrt{\frac{5\mu_n(W/L)_{1,2}}{\mu_p(W/L)_{3,4}}} \quad (30)$$

# $A_{DM}$ with MOS Loads ( $\lambda \neq 0, \gamma \neq 0$ )




$$V_{out1} = -g_{m1,2}(r_{o1,2} \parallel r_{o3,4})\frac{v_d}{2} \quad (31)$$

$$V_{out2} = -g_{m1,2}(r_{o1,2} \parallel r_{o3,4})\left(-\frac{v_d}{2}\right) \quad (32)$$

$$A_{DM} = \frac{V_{out1} - V_{out2}}{v_d} \quad (33)$$

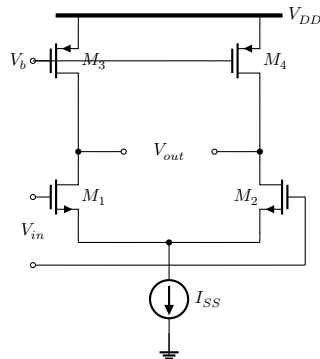
$$= -g_{m1,2}(r_{o1,2} \parallel r_{o3,4}) \quad (34)$$


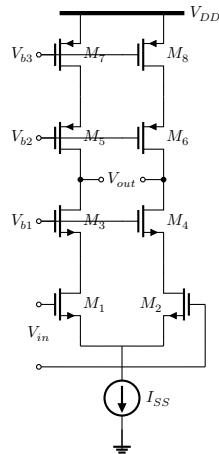
# $A_{DM}$ with MOS Loads ( $\lambda \neq 0, \gamma \neq 0$ )



Higher  $R_{out}$   
→ High  $A_{DM}$   
→ Small  $V_{in,CM}$  headroom  
Telescopic cascode



# $A_{DM}$ with MOS Loads ( $\lambda \neq 0, \gamma \neq 0$ )




$$V_{out1} \cong -g_{m1,2} \{ [r_{o1,2} + r_{o3,4} + (g_{m3,4} + g_{mb3,4})r_{o3,4}r_{o1,2}] \parallel [r_{o7,8} + r_{o5,6} + (g_{m5,6} + g_{mb5,6})r_{o5,6}r_{o7,8}] \} \frac{v_d}{2} \quad (35)$$



$$V_{out2} \cong -g_{m1,2} \{ [r_{o1,2} + r_{o3,4} + (g_{m3,4} + g_{mb3,4})r_{o3,4}r_{o1,2}] \parallel [r_{o7,8} + r_{o5,6} + (g_{m5,6} + g_{mb5,6})r_{o5,6}r_{o7,8}] \} \left(-\frac{v_d}{2}\right) \quad (36)$$

$$A_{DM} = \frac{V_{out1} - V_{out2}}{v_d} \cong -g_{m1,2} [(g_{m3,4} + g_{mb3,4})r_{o3,4}r_{o1,2} \parallel (g_{m5,6} + g_{mb5,6})r_{o5,6}r_{o7,8}] \quad (37)$$

# $A_{DM}$ with MOS Loads

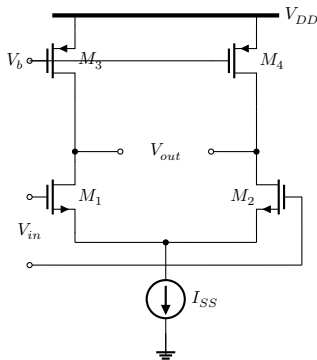

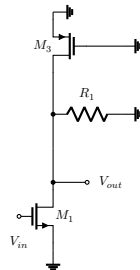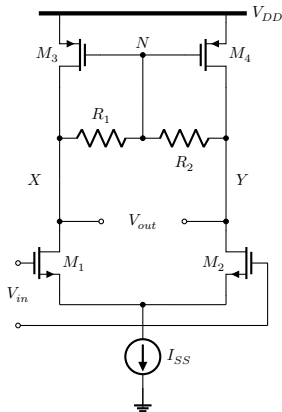
$$A_v = g_{mN} \parallel (r_{ON} r_{OP}) \quad (38)$$



$$|A_v| = g_{m1} (r_{O1} \parallel R_1 \parallel r_{O3}) \quad (39)$$



## Current Defined by Resistors

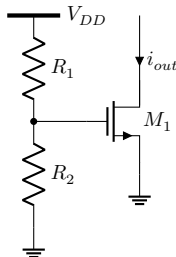

- $I_{out}$  loosely defined.


If  $\lambda = 0$

$$I_{out} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left( \frac{R_2}{R_1 + R_2} V_{DD} - V_{TH1} \right)^2 \quad (40)$$

Variations by temperature:  $\mu_n, V_{TH1}$

Variations by process:  $\frac{R_2}{R_1 + R_2}, V_{TH1}$

# Current Mirror

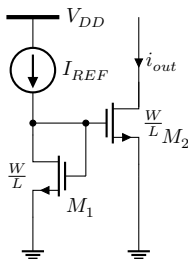

$$I_{out} = \frac{(W/L)_2}{(W/L)_1} I_{REF} \quad (41)$$

- $\mu_n$  and  $V_{TH}$  still vary with temperature, but are canceled out in ratio
- $I_{out}$  precisely defined.

If  $\lambda = 0$

$$I_{REF} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_A - V_{TH1})^2 \quad (42)$$


$$I_{out} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_2 (V_A - V_{TH2})^2$$

$V_{TH1}, V_{TH2}$  : Almost identical if two transistors are drawn close to each other in layout.


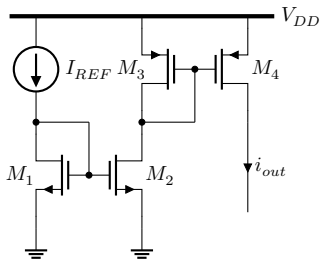
## Current Mirror Examples

Calculate  $I_{out}$  in terms of  $I_{REF}$




$$I_{out} = \frac{(W/L)_2}{(W/L)_1} \frac{(W/L)_4}{(W/L)_3} I_{REF} \quad (43)$$

- DC or small-signal current amplification or reduction can be achieved if transistors are properly ratioed.




## DC Amplification by Current Mirror

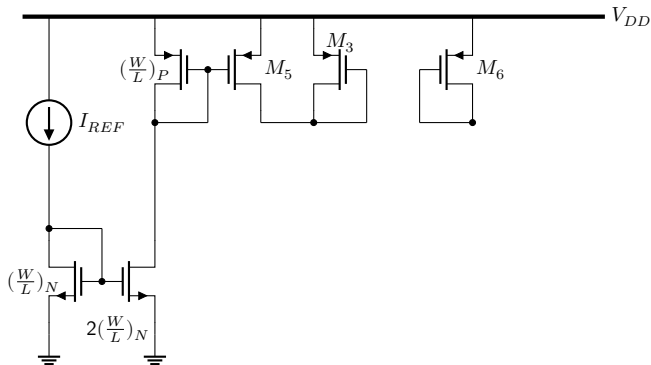

$$A_{\text{DM}} = \frac{v_{\text{out } 1} - v_{\text{out } 2}}{v_d} \approx -\frac{gm_{1,2}}{gm_{3,4}} \approx -\sqrt{\frac{5\mu_n(W/L)_{1,2}}{\mu_p(W/L)_{3,4}}} \quad (44)$$

# Amplification by Current Mirror

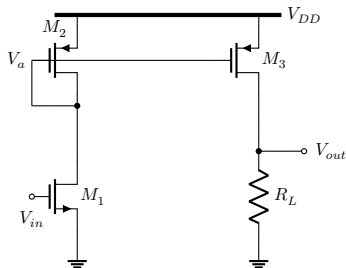

$$v_a = -v_{in} gm_1 (r_{o1} \parallel r_{o2} \parallel \frac{1}{gm_2}) \quad (45)$$

$$v_{out} = -v_a gm_3 (R_L \parallel r_{o3}) \quad (46)$$



$$\frac{v_{out}}{v_{in}} = gm_1 (r_{o1} \parallel r_{o2} \parallel \frac{1}{gm_2}) gm_3 (R_L \parallel r_{o3}) \quad (47)$$

If  $\lambda = \gamma = 0$

$$\frac{v_{out}}{v_{in}} = gm_1 \frac{gm_3}{gm_2} R_L = gm_1 \frac{(W/L)_3}{(W/L)_2} R_L \quad (48)$$




## Differential Pair with Current Mirror

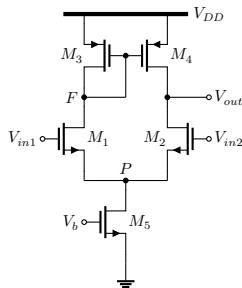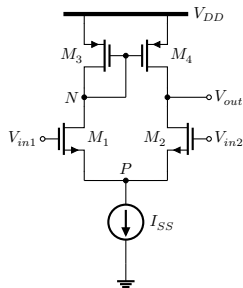

- $V_{in}$  increases
- $I_{D1}, I_{D3}, I_{D4}$  increases
- $I_{D2}$  decreases
- $V_{out}$  increases

- $V_{in1} > V_F + V_{TH1} \rightarrow M_1$  enters into triode
- For  $M_2$  in saturation,  $V_{out} \geq V_{in,CM} - V_{TH2}$

# Differential Pair with Active Load

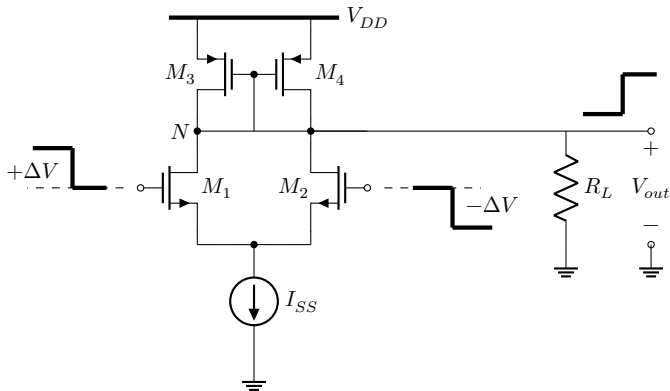

# Asymmetric Differential Pair



Why N is not on the right branch?

Caveat: Because of the vastly different resistance magnitude at the drains of  $M_1$  and  $M_2$ , the voltage swings at these two nodes are different and therefore node P cannot be viewed as a virtual ground when  $V_{in2} = -V_{in1}$ .

