



Lecture 15: Emitter Follower and Common Gate

ECE3110J, Electronic Circuits

Xuyang Lu
2024 Summer



上海交通大學
SHANGHAI JIAO TONG UNIVERSITY

Recap of Last Lecture




- Source Follower

Topic to be covered



- Source Follower
- Emitter Follower
- Common Gate


CS + Source Follower

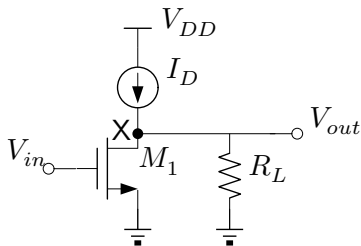

$$A_v = -g_{m1} (r_{o1} \parallel R_L) \quad (1)$$

- Voltage gain severely reduced when R_L very small

CS + Source Follower

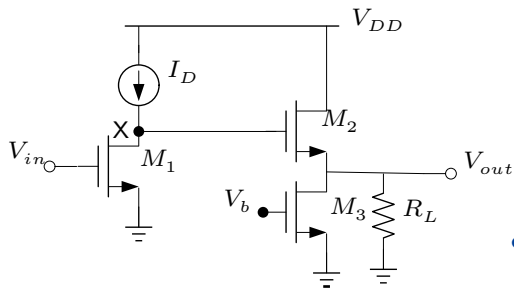

$$A_v = -g_{m1}r_{o1} \times g_{m2} \left(r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \parallel r_{o3} \parallel R_L \right) \quad (2)$$

- Voltage gain maintained when R_L very small

Source Follower Example




$(W/L)_1 = 20/0.5, I_D = 0.2 \text{ mA}, V_{THO} = 0.6 \text{ V},$
 $2\Phi_F = 0.7 \text{ V}, \mu_n C_{ox} = 50 \mu\text{A}/\text{V}^2, \gamma = 0.4 \text{ V}^{1/2}, \lambda = 0$

- Calculate V_{out} for $V_{in} = 1.2 \text{ V}$.

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{THO})^2 \quad (3)$$
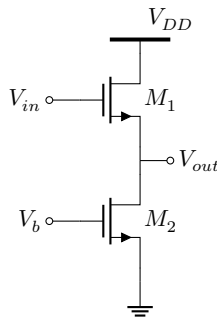
$$\rightarrow V_{out} = 0.153 \text{ V} \quad (4)$$




Source Follower Example



$$V_{TH1} = V_{TH0} + \gamma \left(\sqrt{2\Phi_F + V_{out}} - \sqrt{2\Phi_F} \right) = 0.635 \text{ V} \quad (5)$$
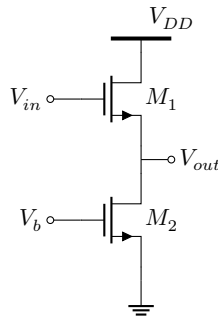
$$\rightarrow V_{out} \approx 0.118 \text{ V} \quad (6)$$




Source Follower Example



- Minimum $(W/L)_2$ for which M_2 remains saturated.

$$V_{out} = 0.118 \text{ V} \geq V_{GS2} - V_{TH2} \quad (7)$$
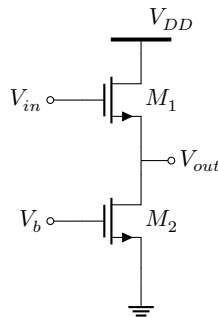
$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS2} - V_{TH2})^2 \rightarrow \left(\frac{W}{L} \right)_2 \geq \frac{283}{0.5} \quad (8)$$



Source Follower Example




Calculate the small signal voltage gain of the circuit below.

$$G_m = g_{m1} \quad (9)$$

$$R_{out} = \frac{1}{g_{m1} + g_{mb1}} \parallel r_{o1} \parallel \frac{1}{g_{m2} + g_{mb2}} \parallel r_{o2} \quad (10)$$


$$A_v = G_m R_{out} \quad (11)$$

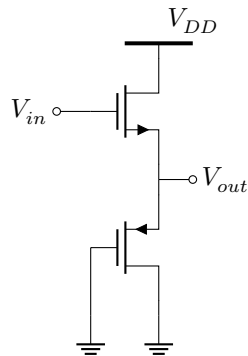

Emitter Follower (Common Collector)



Current Amplifier

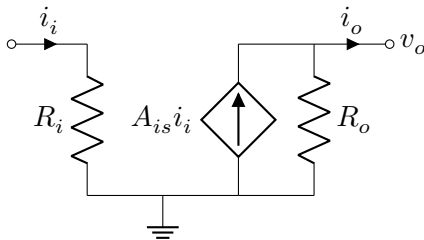


Short-Circuit Current Gain
($R_i = 0, R_o = \infty$)

$$A_{ix} \equiv \left. \frac{i_o}{i_i} \right|_{v_o=0} \text{ (A/A)} \quad (12)$$

- Reading: Sedra & Smith, 8th Ed.: 7.3 (BJT CC)


Transconductance Amplifier

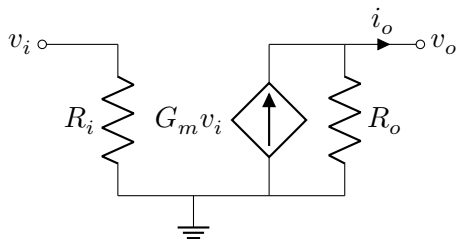

Short-Circuit Transconductance
($R_i = \infty, R_o = \infty$)

$$G_m \equiv \frac{i_o}{v_i} \Big|_{v_o=0} \text{ (A/V)} \quad (13)$$


Transresistance Amplifier

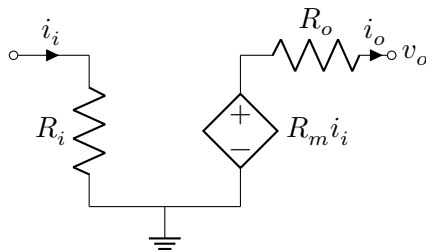

Short-Circuit Transresistance
($R_i = 0, R_o = 0$)


$$R_m \equiv \frac{v_o}{i_i} \Big|_{i_o=0} \text{ (V/A)} \quad (14)$$

Emitter Follower

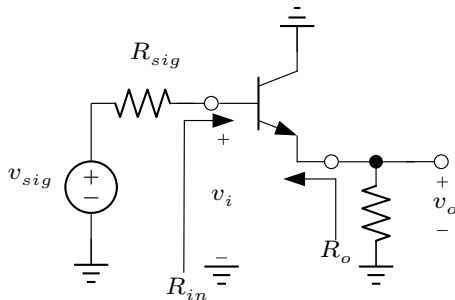


- Transistor is biased to be in the FAR using the same biasing technique for CE amplifier.

Emitter Follower Impedance

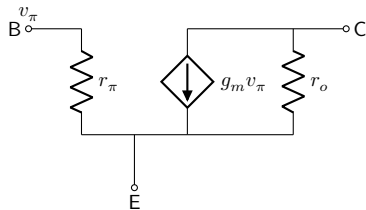

π -model

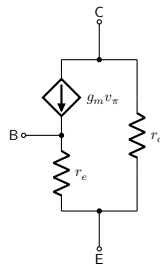


T-model

$$g_m = \frac{\alpha}{r_e} r_\pi = (\beta + 1) r_e \quad (15)$$




Emitter Follower Impedance

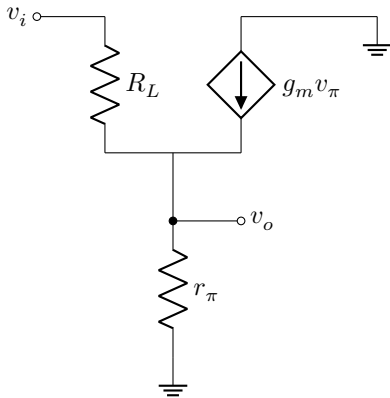

$$R_{in} = r_{\pi} + (\beta + 1)R_L \quad (16)$$

$$R_{out} = r_{\pi} \parallel (1/g_m) \quad (17)$$

Emitter Follower Gain

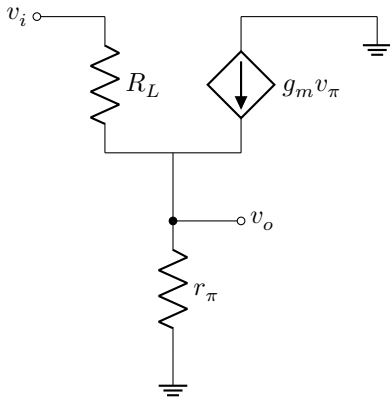


$$\frac{v_o}{v_i} = \frac{R_L}{\frac{1}{g_m + 1/r_\pi} + R_L} \quad (18)$$

CC Amplifier with Biasing Circuit



- No collector resistor
- no bypass capacitor
- Biasing scheme remains the same.
- Output taken out at the emitter.


CC Amplifier with Biasing Circuit

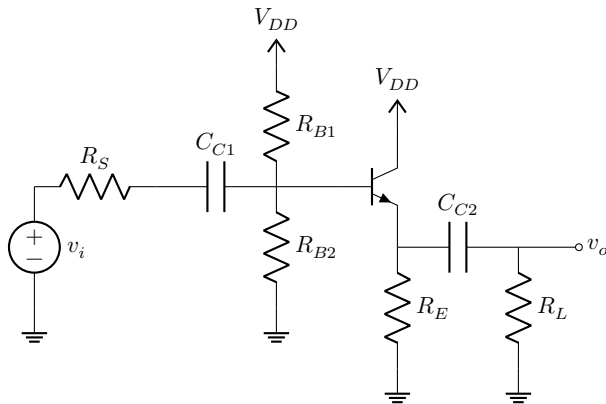


CC Amplifier with Biasing Circuit



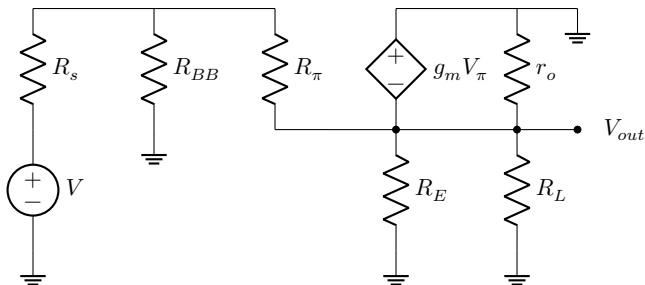Use the current relationship of i_b and i_c



CC Amplifier with Biasing Circuit

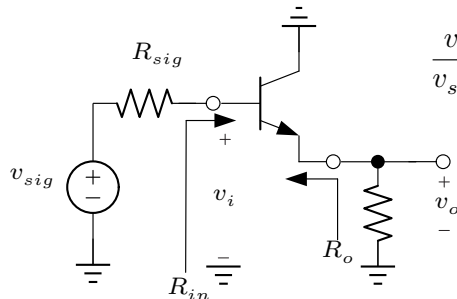


$$\frac{v_i}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} = \frac{(\beta + 1)(r_e + R_L)}{(\beta + 1)(r_e + R_L) + R_{sig}} \quad (19)$$

$$G_v \equiv \frac{v_o}{v_{sig}} = \frac{v_i}{v_{sig}} \times A_v \quad (20)$$

$$G_v = \frac{(\beta + 1)R_L}{(\beta + 1)R_L + (\beta + 1)r_e + R_{sig}} \quad (21)$$

CC Amplifier Swing

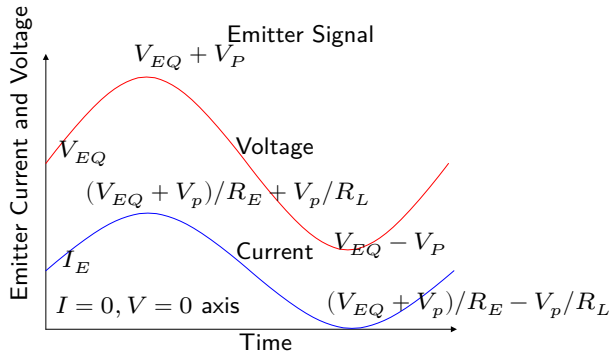

- Assume output is a sinusoid with peak voltage of V_P
- Emitter voltage can get to within $V_{CE,sat}$ of the supply voltage, therefore the maximum output voltage is $V_{CC} - V_{CE,sat} - V_{EQ}$.

CC Amplifier Swing



Total emitter current is given by:

$$i_E = \frac{V_{EQ}}{R_E} + \frac{v_p}{R_E} + \frac{v_p}{R_L} \quad (22)$$

$$i_E = \frac{V_{EQ}}{R_E} - \frac{V_P}{R_E} - \frac{V_P}{R_L} = 0 \quad (23)$$

$$\frac{V_{EQ}}{R_E} - \frac{V_P(R_L + R_E)}{R_L R_E} = 0 \quad (24)$$





CC Amplifier Swing



$$V_P = \frac{V_{EQ}(R_L)}{R_L + R_E} = \frac{V_{EQ}}{\left(1 + \frac{R_E}{R_L}\right)} \quad (25)$$





$$V_{E\min} = V_{EQ} - V_P = \frac{V_{EQ}(R_E)}{R_L + R_E} = \frac{V_{EQ}}{\left(1 + \frac{R_L}{R_E}\right)} \quad (26)$$

Ideal Amplifier: Voltage Amp. and Transimpedance Amp.

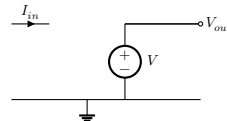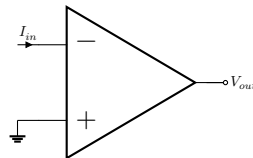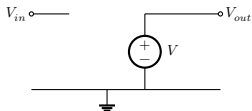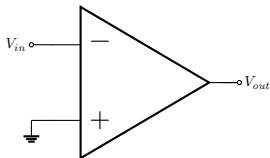上海交通大学
SHANGHAI JIAO TONG UNIVERSITY


- For driving a low impedance load, source follower, as a buffer, provides no gain but large input impedance and low output impedance.

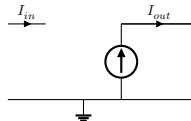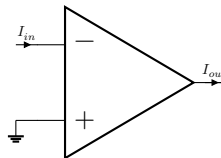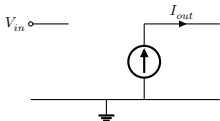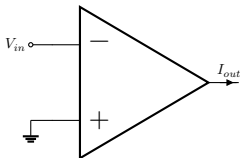Ideal Amplifier: Transconductance Amp. and Current Amp.



- For driving a low impedance load, source follower, as a buffer, provides no gain but large input impedance and low output impedance.

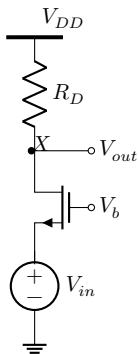
Common-Gate ($\lambda = 0, \gamma \neq 0$)



- $V_{in} > V_b - V_{TH} \rightarrow M_1 \text{ Off}$
- $V_{out} = V_{DD}$
- $V_b - V_{TH} > V_{in} > V_{in1} \rightarrow M_1 \text{ in Saturation}$

$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2 \quad (27)$$

Common-Gate

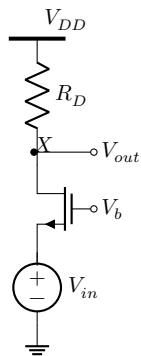

At the boundary of triode/saturation:

$$V_{out} = V_b - V_{TH} \quad (28)$$

$$= V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in1} - V_{TH})^2 \quad (29)$$

$$V_{in} < V_{in1} \rightarrow M_1 \text{ in Triode} \quad (30)$$

Triode region equation as follows:

$$V_{out} = V_{DD} - R_D \mu_n C_{ox} \frac{W}{L} \left[(V_b - V_{in} - V_{TH}) (V_{out} - V_{in}) - \frac{1}{2} (V_{out} - V_{in})^2 \right] \quad (31)$$

Common-Gate ($\lambda = 0, \gamma \neq 0$)



$$V_b - V_{TH} > V_{in} > V_{in1} \rightarrow M_1 \text{ in Saturation} \quad (32)$$

$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2 \quad (33)$$



$$\frac{\partial V_{out}}{\partial V_{in}} = -R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} 2 (V_b - V_{in} - V_{TH}) \left(-1 - \frac{\partial V_{TH}}{\partial V_{in}} \right) \quad (34)$$

$$= R_D \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH}) \left(1 + \frac{\partial V_{TH}}{\partial V_{in}} \right) \quad (35)$$

$$A_v = \frac{\partial V_{out}}{\partial V_{in}} = R_D g_m (1 + \eta) \quad (36)$$

- g_m is a function of I_D and η is a function of V_{SB} .
- A_v is not quite linear.

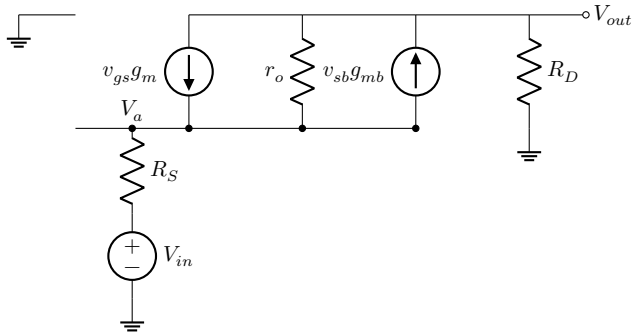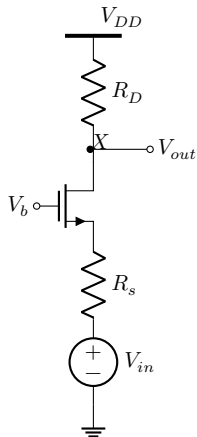Common-Gate ($\lambda = 0, \gamma \neq 0$ Small-signal)



Common-Gate ($\lambda = 0, \gamma \neq 0$ Small-signal)



$$G_m = \frac{(g_m + g_{mb})r_o + 1}{r_o + R_S + (g_m + g_{mb})r_o R_S} \quad (37)$$


$$R_{\text{out}} = R_D \parallel [r_o + R_S + (g_m + g_{mb})r_o R_S] \quad (38)$$

$$A_v = \frac{(g_m + g_{mb})r_o + 1}{r_o + R_S + (g_m + g_{mb})r_o R_S + R_D} R_D \approx R_D g_m (1 + \eta) \quad (39)$$

$$\text{If } R_S = 0 \quad \text{and} \quad r_o = \infty \quad (40)$$

Common-Gate SS gain

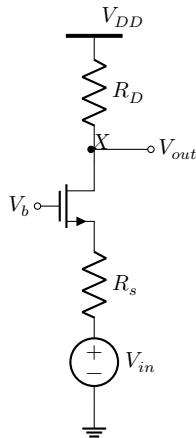Transconductance gain: use Norton equivalent



Common-Gate SS gain



Output Impedance: SS model