



Lecture 11: Mosfet Large Signal

VE311 Electronic Circuits

Xuyang Lu
2024 Summer



上海交通大學
SHANGHAI JIAO TONG UNIVERSITY

Recap of Last Lecture



- MOSFET

Topics to Be Covered



- MOSFET Circuits

Spice Models



NMOS Model

LEVEL=1	VTO=0.7	GAMMA=0.45	PHI=0.9
NSUB=9e+14	LD=0.08e-6	UO=350	LAMBDA=0.1
TOX=9e-9	PB=0.9	CJ=0.56e-3	CJSW=0.35e-11
MJ=0.45	MJSW=0.2	CGDO=0.4e-9	JS=1.0e-8

PMOS Model

LEVEL=1	VTO=-0.8	GAMMA=0.4	PHI=0.8
NSUB=5e+14	LD=0.09e-6	UO=100	LAMBDA=0.2
TOX=9e-9	PB=0.9	CJ=0.94e-3	CJSW=0.32e-11
MJ=0.5	MJSW=0.3	CGDO=0.3e-9	JS=0.5e-8

Spice Models



- Simulators such as SPICE and Cadence need accurate models for each device.
- Above is the simplest MOS SPICE model, known as “Level 1,” and provide typical values for each parameter corresponding to 0.5- μm technology.

Spice Models



VTO : threshold voltage with zero V_{SB} (unit : V)

GAMMA : body effect coefficient (unit : $V^{1/2}$)

PHI : $2\Phi_F$ (unit : V)

TOX : gate oxide thickness (unit : m)

NSUB : substrate doping (unit : cm^{-3})

LD : source/drain side diffusion (unit : m)

UO : channel mobility (unit : $cm^2/V/s$)

LAMBDA : channel-length modulation coefficient (unit : V^{-1})

Spice Models



CJ : source/drain bottom-plate junction capacitance per unit area (unit : F/m^2)

CJSW : source/drain sidewall junction capacitance per unit length (unit : F/m)

PB : source / drain junction built-in potential (unit : V)

MJ : exponent in CJ equation (unitless)

MJSW : exponent in CJSW equation (unitless)

CGDO: gate-drain overlap capacitance per unit width (unit : F/m)


CGSO : gate-source overlap capacitance per unit width (unit : F/m)

JS : source/drain leakage current per unit area (unit : A/m^2)

Body Effect Example


 
$$\lambda \neq 0 \quad \gamma \neq 0 \quad (1)$$



$$\left(\frac{W_{drawn}}{L_{drawn}}\right) = \frac{10\mu m}{2\mu m} \quad (2)$$


$$V_{th} = 0.7 + 0.45(\sqrt{0.9 + 1} - \sqrt{0.9}) \quad (3)$$

$$I_D = \frac{1}{2}\mu_n C_{ox} \left(\frac{W}{L_{eff}}\right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}) \quad (4)$$



Body Effect Example
 
$$\lambda \neq 0 \quad \gamma \neq 0 \quad (5)$$



$$\left(\frac{W_{drawn}}{L_{drawn}}\right) = \frac{10\mu m}{2\mu m} \quad (6)$$



$$V_{th} = 0.7 + 0.45(\sqrt{0.9 + 1} - \sqrt{0.9}) \quad (7)$$

$$I_D = \frac{1}{2}\mu_n C_{ox} \left(\frac{W}{L_{eff}}\right) [(V_{GS} - V_{TH}) V_{DS} - \frac{1}{2}V_{DS}^2] \quad (8)$$

Body Effect Example





  Sketch I_D as a function of V_X increasing from $-\infty$ to 0. Assume $V_{TH} = 0.6V$, $\gamma = 0.4V^{1/2}$ and $2\Phi_F = 0.7V$.





Solution: $1.2 = 0.6 + 0.4 (\sqrt{0.7 - V_X} - \sqrt{0.7})$, $V_X = -4.76 V$

Drain-induced Barrier Lowering

  




In short-channel devices, the drain is close enough to gate the channel, and so a high drain voltage can open the bottleneck and turn on the transistor prematurely.

Drain-induced Barrier Lowering

  


In short-channel devices, the drain is close enough to gate the channel, and so a high drain voltage can open the bottleneck and turn on the transistor prematurely.

NMOS vs PMOS

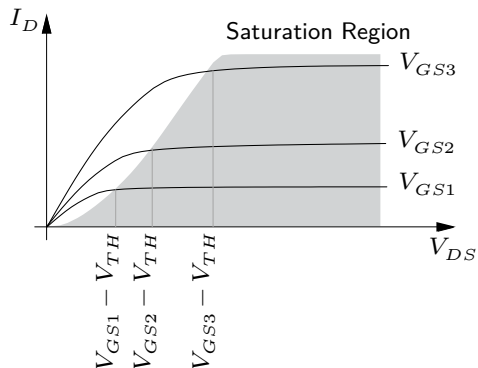  


PMOS Example

 

Small-Signal Example


 
$$\left(\frac{W_{drawn}}{L_{drawn}}\right) = \frac{10\mu m}{2\mu m} \quad (9)$$




- No bulk connect means ground for NMOS

Transconductance



 - For the NMOS operating in the saturation region ($V_{DS} \geq V_{GS} - V_{TH}$):



$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L'} (V_{GS} - V_{TH})^2 \quad (10)$$

- ΔV_{GS} results in $\Delta I_D = g_m \times \Delta V_{GS}$.

Transconductance





$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L'} (V_{GS} - V_{TH}) = \sqrt{2\mu_n C_{ox} \frac{W}{L'} I_D} = \frac{2I_D}{V_{GS} - V_{TH}} \quad (11)$$

With channel-length modulation




$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) (1 + \lambda V_{DS}) \quad (12)$$

$$= \sqrt{2\mu_n C_{ox} (W/L) I_D} (1 + \lambda V_{DS}) \quad (13)$$

Transconductance

  

Transconductance

   

- For a given NMOS, g_m changes according to the DC biasing condition.
- If a small signal is applied to a NMOS with defined biasing values, we assume the signal amplitude is small enough that the variation in g_m is negligible.


Small-Signal Model for NMOS




$$r_o = \frac{\partial V_{DS}}{\partial I_D} \quad (14)$$

$$= \frac{1}{\partial I_D / \partial V_{DS}} \quad (15)$$
 
$$= \frac{1}{\frac{1}{2}\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \cdot \lambda} \quad (16)$$



Small-Signal Model for NMOS

 

Small-Signal Model for NMOS



$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}} \quad (17)$$

$$= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \left(-\frac{\partial V_{TH}}{\partial V_{BS}} \right) \quad (18)$$


$$\frac{\partial V_{TH}}{\partial V_{BS}} = -\frac{\partial V_{TH}}{\partial V_{SB}} \quad (19)$$

$$= -\frac{\gamma}{2} (2\Phi_F + V_{SB})^{-1/2} \quad (20)$$


$$g_{mb} = g_m \frac{\gamma}{2\sqrt{2\Phi_F + V_{SB}}} \quad (21)$$

$$= \eta g_m \quad (22)$$

Small-Signal Model for NMOS

 

 
$$\downarrow i_d = g_m \cdot v_{gs} \quad \uparrow i_d = g_{mb} \cdot v_{sb} \quad (23)$$



Small-Signal Example


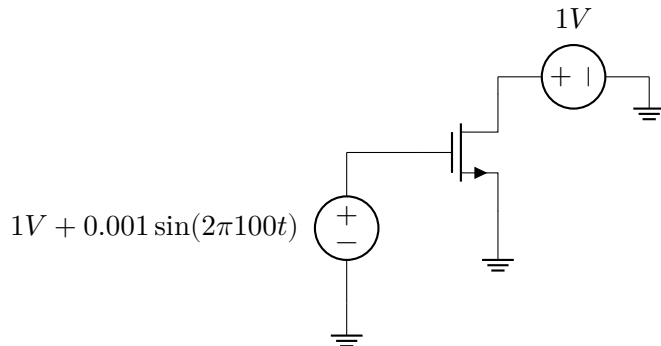
$$\left(\frac{W_{drawn}}{L_{drawn}}\right) = \frac{10 \mu m}{2 \mu m} \quad (24)$$




Small-Signal Example



$$\left(\frac{W_{drawn}}{L_{drawn}}\right) = \frac{10 \mu m}{2 \mu m} \quad (25)$$


$$1V + 0.001 \sin(2\pi 100t)$$

 


Small-Signal Example



 
$$\left(\frac{W_{drawn}}{L_{drawn}}\right) = \frac{10 \mu m}{2 \mu m} \quad (26)$$



Small-Signal Model for PMOS

 

 
$$\uparrow i_d = g_m \cdot v_{gs} \quad \downarrow i_d = g_{mb} \cdot v_{sb} \quad (27)$$




Layout



NMOS

 

PMOS

 

Layout




- W/L is chosen to determine g_m .
- Minimum L is dictated by the process.
- Design rules:
 - Poly-Si extends beyond the channel area by some amount.
 - Enough n^+ , p^+ or poly-Si area surrounding each via.
 - Enough distance between two vias.
 - Many others.

NMOS vs PMOS in Performance




- PMOS devices are quite inferior to NMOS in most CMOS technology.
- Lower mobility of holes ($\mu_p C_{ox} \approx 0.5 \mu_n C_{ox}$) yield lower current drive and conductance.
- NMOS exhibit higher output resistance, providing more ideal current sources and higher voltage gain.
- It is preferable to use NMOS rather than PMOS wherever possible.

Common-Source

 

$$V_{in} = 0.8 + 0.001 \sin(2\pi 100t) \quad (28)$$

Common-Source

 

$$V_{in} = 4.1 + 0.001 \sin(2\pi 100t) \quad (29)$$